

**CTEVT, DIPLOMA**

# **Question Bank Of Electrical Engineering 2071 To 2079**

**Website:- [www.arjun00.com.np](http://www.arjun00.com.np)**

**Regular/ Back Exam 2071, Bhadra/Ashwin**

**Program : Diploma in Information Technology Full Marks: 80**  
**(IT)/ Computer Engineering (New)**

**Year/ Part : I/II Pass Marks: 32**

**Subject : Electrical Engineering Time: 3 hrs.**

---


*Candidates are required to give their answers in their own words as far as practicable. The figures in the margin indicate full marks.*

**Attempt (Any Eight) Questions.**


1. Define the following: [5x2=10]
  - (a) Magnetic flux density
  - (b) Frequency
  - (c) Instantaneous value of alternating quantity
  - (d) Lenz's Law
  - (e) Electric power
2. Define and explain Faraday's law of electromagnetic induction. [10]
3. In a RLC series circuit consists of a resistance of  $8\Omega$ , inductance of  $0.15H$  and capacitance of  $125\mu F$ . If voltage of  $230V$ ,  $50Hz$  supply is applied. Calculate [10]
  - (a) Impedance
  - (b) Current
  - (c) Power factor
  - (d) Voltage across each element.



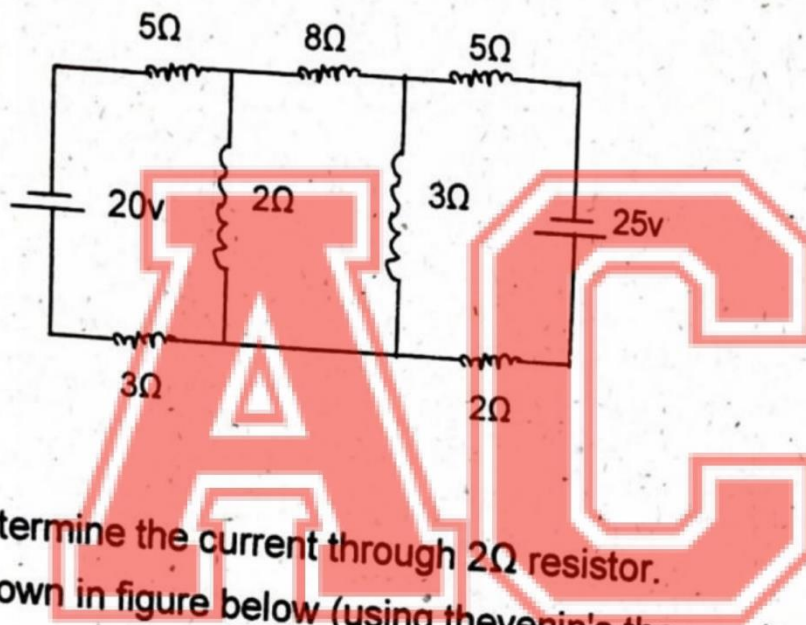4. What are the advantages of 3- $\phi$  system? Differentiate between generator and motor. [7+3=10]
5. Explain the construction and working principle of 3 phase induction motros. [10]
6. Using nodal analysis. Find the current through  $8\Omega$  register shown in network below. [10]




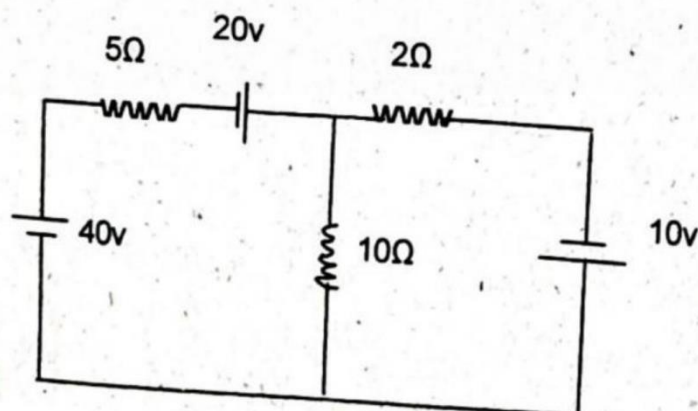7. Determine the current through  $2\Omega$  resistor. Shown in figure below (using thevenin's theorem). [10]



8. Using mesh analysis. Find the current flowing in branch AB and BC in circuit shown below.

[10]

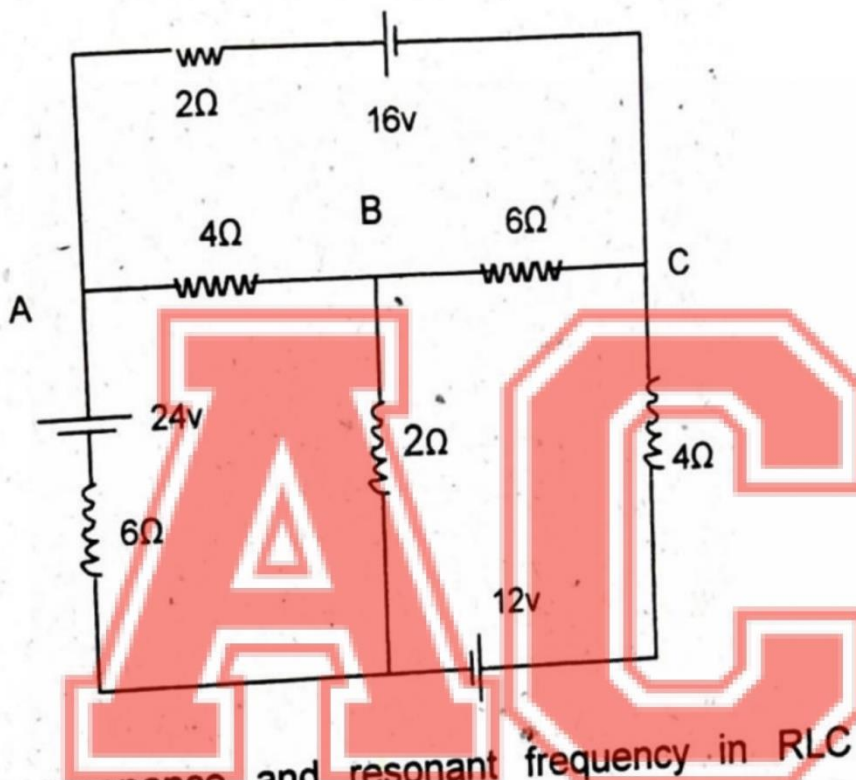

9. Define resonance and resonant frequency in RLC series circuit. Derive the resonant frequency Expression.

[10]

10. Write short notes on (Any two)

[2x5=10]

- (a) Single phase ac motor
- (b) Primary and secondary cell
- (c) Charging methods of battery.





Council for Technical Education and Vocational Training  
**Office of the Controller of Examinations**  
Sanothimi, Bhaktapur

**Regular/Back Exam-2073 Bhadra/Ashwin**

**Program: Diploma in Information Technology  
/Computer Engineering**

**Full Mark: 80**

**Year/Part: I/II (New Course)**

**Pass Mark: 32**

**Subject: Electrical Engineering**

**Time: 3 hrs.**


**Candidates are required to give their answers as practicable. The figures in the margin are for guidance only.**




[www.arjun00.com.np](http://www.arjun00.com.np)

**Attempt Any Five Questions.**

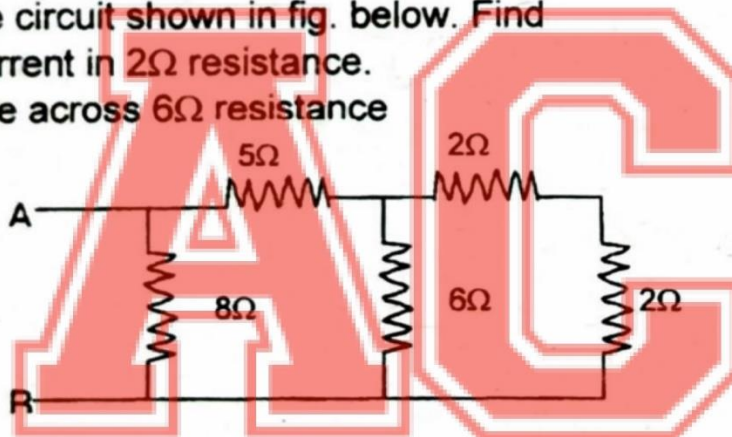
1. a) State and explain faraday's law of electromagnetic induction? [4]  
b) What do you mean by Magnetic field intensity? [2+5=6]  
Give the B.H. curve of a magnetic material and explain the various parts of the curve.  
c) A battery of 24V is applied across terminal AB of the circuit shown in fig. below. Find [6]  
i) The current in  $2\Omega$  resistance.  
ii) Voltage across  $6\Omega$  resistance



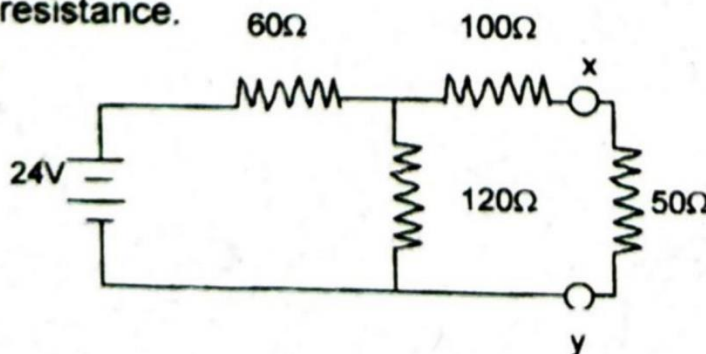2. a) State and explain maximum power transfer theorem and prove that efficiency under maximum power transfer condition is 50%. [3+2=5]  
b) Find Thevenin Equivalent circuit to the left of terminal x-y in figure below and find the value of current flowing through  $50\Omega$  resistance. [3+3=6]



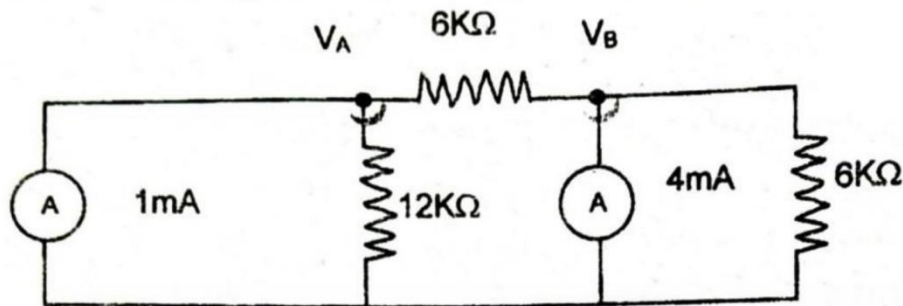c) Solve the circuit shown in figure below using nodal analysis and find  $V_A$  and  $V_B$  [5]



3. a) What do you mean by transformer? Explain the working principle of single phase transformer. [2+6=8]  
b) Explain the construction and working principle of 3 $\phi$  induction motor in brief. [4+4=8]
4. a) What do you mean by cell? Explain construction and chemical reaction during charging of lead acid cell. [2+6=8]  
b) In RLC series resonance circuit  $R=16\Omega$ ,  $L=20\text{mH}$ , and  $C=0.01\mu\text{F}$ . If the applied voltage is 4V. find [8]  
i) The frequency at which circuit p.f. is equal to 1.  
ii) Circuit current during resonance  
iii) Voltage drop across inductance  
iv) Quality Factor.
5. a) Explain the advantage of 3 phase system over single phase system. [6]  
b) Explain and derive the relation between  $V_L$ ,  $V_{Ph}$  and  $I_L$ ,  $I_{Ph}$  in star connection using phasor diagram [10]
6. Write short notes on: (Any Four) [4x4=16]  
a) Mercury cell  
b) DC motor  
c) power in AC circuit  
d) Super position theorem  
e) Capacitor and inductor

Good Luck!



[www.arjun00.com.np](http://www.arjun00.com.np)



Council for Technical Education and Vocational Training  
Office of the Controller of Examinations  
Sanothimi, Bhaktapur  
Regular/Back Exam-2074, Shrawan/Bhadra

|            |                                                |                |
|------------|------------------------------------------------|----------------|
| Program:   | Diploma in Computer and Information Technology | Full Marks: 80 |
| Year/Part: | I/II [New Course]                              | Pass Marks: 32 |
| Subject:   | Electrical Engineering                         | Time: 3:00 hrs |

Candidates are required to give their practicable. The figures in the margin



[www.arjun00.com.np](http://www.arjun00.com.np)

Attempt Any Five Questions

1. Define (Any Five)

[5x2=10]

- |                   |                     |                    |
|-------------------|---------------------|--------------------|
| i) Magnetic field | iii) Flux density   | v) Frequency       |
| ii) Magnetic flux | iv) Field intensity | vi) Electric power |

b) Define and explain Faraday law of electro-magnetic induction.


[6]

2. a) State and explain Ohm's law with suitable example.

[5]

b) Determine the current flowing through  $3\Omega$  resistor in the network shown below using Thevenin's theorem.

[6]

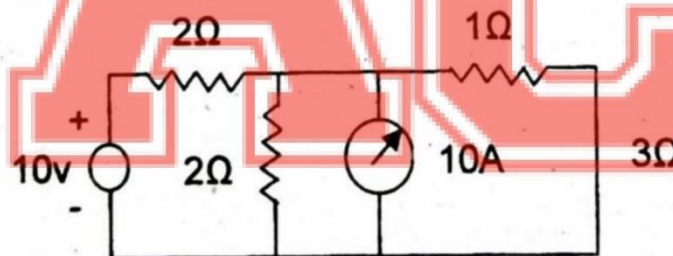


c) State and explain superposition theorem.

[5]

3. a) Using nodal analysis, write down node voltage equation for the circuit to find the current through  $25\Omega$  branch.

[5]

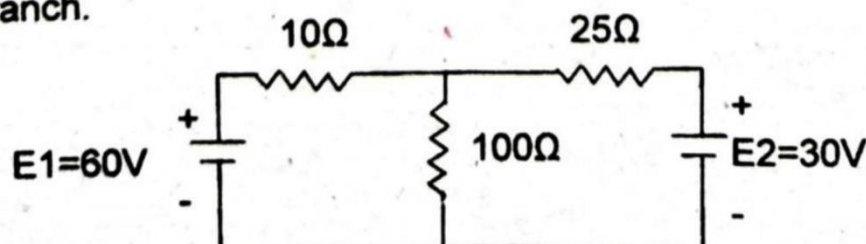

b) An alternating current  $i$  is given by  $i = 141.4 \sin 314t$ . [5]

Find i) The Maxim Value


ii) Frequency

iii) Time period

iv) Instantaneous Value when  $t$  is 3ms

c) A battery of 24V is applied across terminal AB of the circuit shown in figure below. Find: [6]

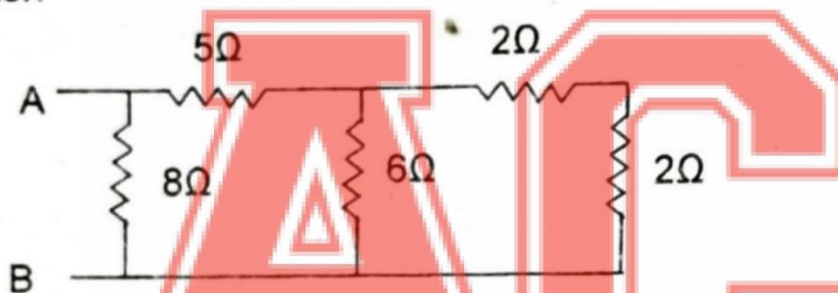i) The current in  $2\Omega$  resistor ii) Voltage across  $6\Omega$  resistor.



4. a) Explain the construction and working principle of single phase transformer. [8]

b) Explain the construction and principle of  $3\phi$  Induction motor in brief. [4+4=8]

5. a) A coil of resistance  $100\Omega$  and inductance  $100H$  is connected in series with a  $100F$  capacitor. The circuit is connected to a  $10V$  variable frequency supply. [8]

Calculate: i) the resonance frequency

ii) Current at resonance

iii) Voltage across  $L$  and  $C$  at resonance.

iv)  $Q$  factor of the circuit.

b) What are the advantages of  $3\phi$  system? Explain about the star and delta connection of  $3\phi$  system. [3+5=8]

6. Write short notes on: (Any Four) [4x4=16]

a) Hysteresis loop

b) Dry cell

c) Series and parallel connection of cell

d) Resonance in RLC series circuit

e) KCL and KVL

f) Single phase AC motor

**Good Luck!**





Council for Technical Education and Vocational Training  
Office of the Controller of Examinations  
Sanothimi, Bhaktapur

**Regular/ Back 2075 Shrawan / Bhadra**

**Program: Diploma in Computer Engineering / Information Technology.** **Full Marks: 80**

**Year/ Part: I/II(New + IT Old Course)**

**Pass Marks: 32**

**Subject: Electrical Engineering**

**Time: 3 hrs.**


Candidates are required to give the answers as far as practicable. The figures in the margin indicate the marks for each question.




[www.arjun00.com.np](http://www.arjun00.com.np)

**Attempt (Any Five) Questions.**

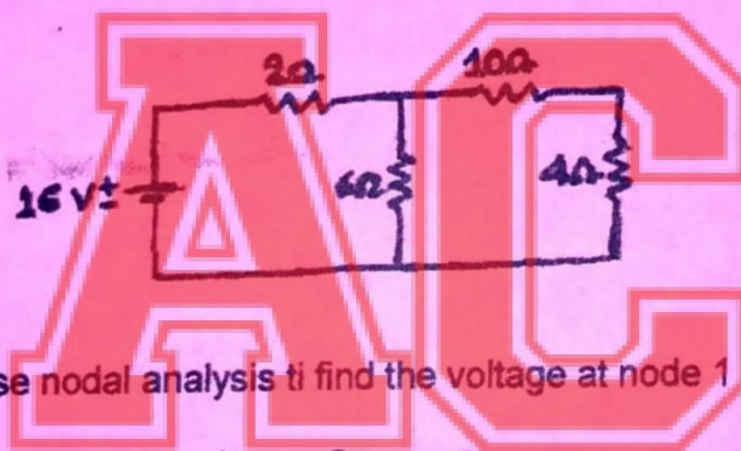1. (a) State and prove maximum power transfer theorem. [8]  
(b) Explain Faraday law of electromagnetic induction. [8]  
What is statically and dynamically induce EMF .
2. (a) Find Thevenins equivalent circuit across  $4\Omega$  and value of current flowing through  $4\Omega$  resistance. [8]



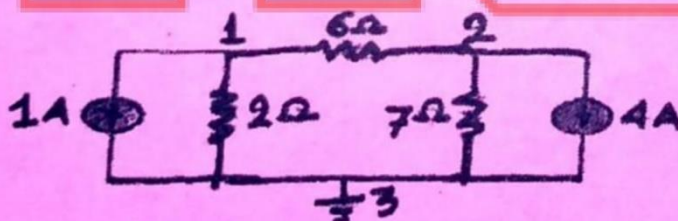- (b) Use nodal analysis to find the voltage at node 1 and 2 [8]



3. (a) What are the advantages of three phase system over single phase system? [8]  
(b) Explain star and delta connection with neat diagram. [8]
4. (a) Explain the construction and working principle of single phase transformer. [8]  
(b) Explain the construction and working principle of three phase induction motor. [8]
5. (a) Define and derive resonant frequency. [8]

Contd.....



(b) What is electrical circuit? what are the different between electrical circuit and magnetic circuit?

[8]

Write short notes on: ( Any four)

[4x4]

- a) Primary and secondary cell.
- b) Single phase AC motor.
- c) Magnetic field intensity.
- d) Resistance.
- e) Average value.

**Good luck !**



[www.arjun00.com.np](http://www.arjun00.com.np)

Council for Technical Education and Vocational Training

Office of the Controller of Examinations

Sanothimi, Bhaktapur

Regular/Back Exam-2076, Shrawan/Bhadra

Program: Diploma in Computer /IT Engineering

Full Marks: 80

Year/Part: II / II (2018, 2010 & IT 2008)

Pass Marks: 32

Subject: Electrical Engineering

Time: 3 hrs


Candidates are required to give their answers in their own words as far as practicable. The figures in the margin indicate the marks.




[www.arjun00.com.np](http://www.arjun00.com.np)

Attempt **Any Eight** questions.

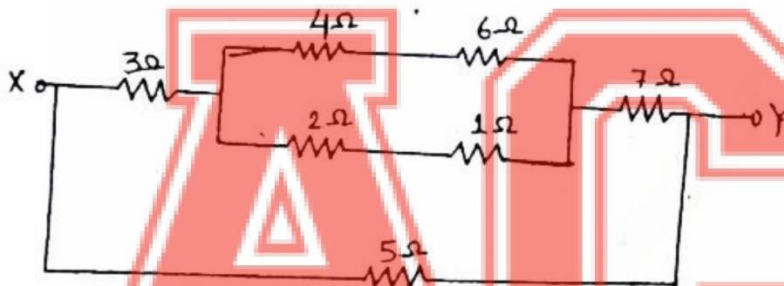- 1.a) Define magnetic material. Differentiate between soft and hard magnetic material. Also explain about Hysteresis loop. 1+4+3]
- b) State and explain Kirchhoff's current and voltage law with necessary clear diagram. [8]
- 2.a) Explain Lenz's law and also calculate the equivalent resistance of the network given in figure : [8]



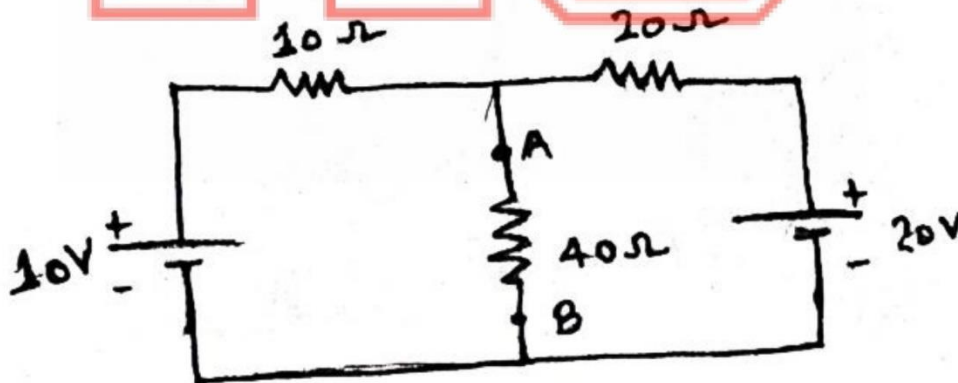- b) Find Thevenin's equivalent circuit across  $40\Omega$  and value of current flowing through  $40\Omega$  resistance of figure: [8]



- 3.a) Explain the phasor representation of single phase AC. [4+4]  
Explain the use of J operator in AC analysis.

Contd.....



- b) Explain the Maximum power transfer theorem with your own example and necessary diagram. [8]
- 4.a) Explain the construction and working principle of single phase AC motor. [8]
- b) Explain the construction and working principle of three phase induction motor. [8]
- 5.a) Write down the advantages of 3-phase system over single phase system. [8]
- b) Differentiate between primary and secondary cells. Define the internal resistance of a cell. [6+2]
6. Write Short Notes on: (Any Four) [4x4= 16]
- a) Single phase Transformer
  - b) RMS value
  - c) Magnetic flux and flux density
  - d) Faraday's law of Induction
  - e) Mercury cell
  - f) Ohm's law

**Good Luck!**



**[www.arjun00.com.np](http://www.arjun00.com.np)**

|            |                                    |                |
|------------|------------------------------------|----------------|
| Program:   | Diploma in Computer/IT Engineering | Full Marks: 80 |
| Year/Part: | I/II (2018, 2013, 2008)            | Pass Marks: 32 |
| Subject:   | Electrical Engineering             | Time: 3 hrs    |


Candidates are required to give their answers in the  
The figures in the margin indicate full marks.



[www.arjun00.com.np](https://www.arjun00.com.np)

**Attempt Any Five questions.**

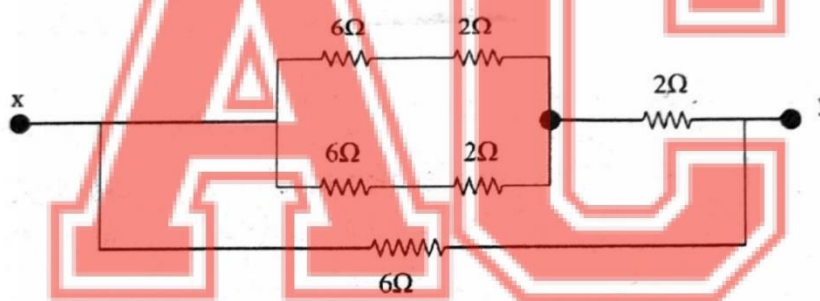1. a) Define the terms: [2+2+2+2=8]
  - i) Magnetic field
  - ii) Magnetic flux
  - iii) Magnetic field intensity
  - iv) Magnetic permeability
- b) Define electric current and voltage. Explain the active and passive electric component. [4+4=8]
2. a) State and Explain the Ohm's law. Calculate the equivalent resistance of the network given in figure : [4+4=8]



Website:- <https://www.arjun00.com.np>

- b) Explain Faraday's Law of Electromagnetic Induction with necessary diagram. [8]
3. a) Explain the generation process of Cc. Define the term Average value and RMS value. [4+2+2=8]
- b) State and Explain the superposition theorem with necessary diagram and example. [8]
4. a) Explain the construction and working principle of single phase transformer. [8]
- b) Explain the construction and working principle of three phase induction motor. [8]

Cont.....



Website:- <https://www.arjun00.com.np>

5. a) Explain the construction and chemical reaction during charging and discharging of Lead acid cell. [8]  
b) Explain the star and Delta Connection of 3-phase source and Load Circuit in brief. [8]
6. **Write short notes on : (Any Four)** [4x4=16]  
a) Norton's Theorem  
b) Hysteresis Loop  
c) Capacitance  
d) J-operator  
e) Electric power and energy  
f) Dry cell

**Good Luck !**

Website:- <https://www.arjun00.com.np>

Website:- <https://www.arjun00.com.np>

Council for Technical Education and Vocational Training  
**Office of the Controller of Examinations**  
Sanothimi, Bhaktapur

**Regular/Back Exam-2078, Magh/Falgun**

**Program: Diploma in Computer/ IT Engineering**

**Full Marks:80**

**Year/ Part: I/II (2018, 2013, 2008 New+Old)**

**Pass Marks: 32**

**Subject: Electrical Engineering**

**Time: 3 hrs.**

Candidates are required to give their answers in their own words as far as possible. The figures in the margin indicate full marks.



[www.arjun00.com.np](https://www.arjun00.com.np)

**Attempt Any Five Questions.**

1. a) Show the analogy between magnetic circuit and electric circuit. State and explain Kirchhoff's law. [4+4]  
b) State Thevenin's theorem. State and explain Norton's theorem with necessary expression and diagram. [2+6]
2. a) Define following terminology: [2x4=8]  
i) Instantaneous values ii) RMS values  
iii) Active power iv) Power factor  
b) State and explain the maximum power transfer theorem. [8]
3. a) A 230V, 50HZ ac supply is applied to a coil of 0.07H inductive and 2.5Ω resistor in series. Calculate the [8]  
i) impedance ii) current iii) phase angle  
iv) power factor Website:- <https://www.arjun00.com.np>  
b) Explain delta connection of 3-phase and also derive the expression for line and phase qualities. [8]
4. a) Define ideal transformer. Explain construction and working principle of single phase transformer. [8]  
b) Define induction motor. Explain construction and working principal of 3-phase induction motor. [2+6]
5. a) Show the final expression for the RLC series circuit. [8]  
b) Define dry cell and mercury cell. Explain series and parallel connection of cell. [3+5]
6. Write short notes on : **(Any Four)** [4x4=16]  
i) Lead acid cell ii) emf  
iii) Single phase AC motor iv) Lenz's law  
v) Generation of sinusoidal EMF

**Good Luck !**

Website:- <https://www.arjun00.com.np>





Program: Diploma in Computer Engineering

Full Marks: 80

Year/Part: I/II (2013, 2018)

© Arjun

Pass Marks: 32

Subject: Electrical Engineering

Time: 3 hrs.


Candidates are required to give their answers in their own words as far as practicable. The figures in the margin indicate full marks.



[www.arjun00.com.np](http://www.arjun00.com.np)

Attempt any **EIGHT** questions.

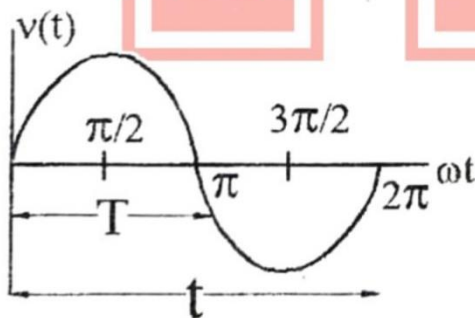1. Define: (any **FIVE**) [5×2]
  - a. Magnetic Flux
  - b. Resistance
  - c. RMS or Effective Value
  - d. Time Period and Frequency
  - e. Electric Power
  - f. Magnetic Field Intensity
  - g. Ohm's Law
2. State Lenz's law. Explain the B-H curve for magnetic materials. [2+8]
3. State Thevenin's Theorem. Explain the procedure for solving the circuit by Thevenin's Theorem. [2+8]
4. Define phasor. Find the average and RMS value of the sine wave as shown below. [2+8]




5. Explain 3-phase system with its advantages and compare star and delta connection with examples. [10]
6. Define ideal transformer. Explain the construction and working principle of single phase transformer. [2+8]
7. With the help of neat diagram, derive the relation between the phase and line current, phase and line voltage in delta connection. [10]

**\*\*Download from [www.arjun00.com.np](http://www.arjun00.com.np)**

Cont. ....

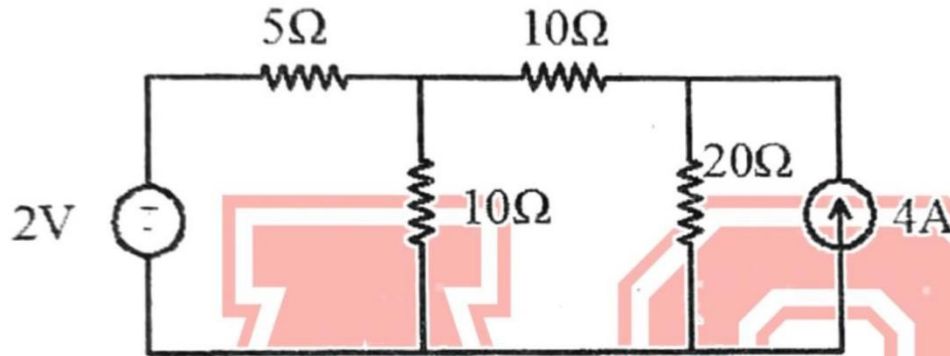8. Define node. Find the current flowing through  $20\Omega$  resistor of the following circuit using nodal analysis. [2+8]



9. Describe primary and secondary cells. Differentiate series and parallel connection of cells. [4+6]
10. Write short notes on: (any **TWO**) [2×5]
- Kirchhoff's Law
  - DC Generator
  - Use of 'J' Operator
  - Dry Cell

*Good Luck !*



[www.arjun00.com.np](http://www.arjun00.com.np)

AC

*\*\*Download from [www.arjun00.com.np](http://www.arjun00.com.np)*