Office of the Controller of Examinations

Sanothimi, Bhaktapur

Regular/Back/Scholarship Exam - 2081/2082 Chaitra/Baishakh

Diploma in Computer Engineering/ Program: Diploma in Information Technology

Full Marks: 80

Year/Part:

II/I (2022) © Arjun

Pass Marks: 32

Subject:

Digital Logic

Time: 3 hrs.

Candidates are required to give their answers in their own words as far as practicable. The figures in the margin indicate full marks. www.arjun00.com.np

Attempt any FIVE questions.

- Define signal. Write down the advantages of digital signal [1+3] 1. over analog signal.
 - b. Convert the following number system:

[4×2]

- i. $(10110.011)_2 = (?)_{10}$
- ii. (3462)₈=(?)₁₆
- iii. (AFCD.2E)16=(?)8
- iv. (69273.58)10=(?)2
- Subtract the following (00110011)₂ from (0110101)₂ using [4] C. 2's complement method.
- Define logic gate. Explain the basic gates with necessary [2+6]a. truth table, symbol and logical expression.
 - State and prove De-Morgan's theorem with necessary truth [5] b. table and diagram.
 - Simplify the following expression using Boolean algebra: [2×1.5] C.
 - x'y + yz' + yz + xy'z' = y + xz'
 - ii. $Y = ABCD + AB\overline{C}D + A\overline{B}C + AC\overline{D}$
- a. Define universal gate. Realize the basic gates using NAND [2+6] gate only with clear figure and truth table.
 - Simplify the following expression using K-map: [4+4]
 - i. $F(A, B, C, D) = \sum m(1, 3, 4, 6, 8, 9, 11, 13, 15) + \sum d(0, 2, 14)$
 - ii. $F(A, B, C, D) = \sum m(3, 5, 7, 8, 10, 11, 12, 13)$

www.arjun00.com.np

Cont.

4.	a.	Define adder. Explain the decimal to BCD encoder with suitable diagram and truth table.	[2+0]
	b.	truth table, diagram and logical expression.	[2+6]
5.	a.	Design JK flip flop with necessary diagram. Explain master slave flip flops.	[6+2]
	b.	Define counter. Explain ripple counter with truth table and waveform.	[2+6]
6.	a.	SISO shift register X-OR gate	[4×4]
	c.	Seven segment display	

Good Luck!

T-flip flop

BCD code

1:4 de-multiplexer

d.

f.





Office of the Controller of Examinations

Sanothimi, Bhaktapur

Regular/Back/Scholarship Exam-2080/2081, Chaitra/Baishakh

Program: Diploma in Computer Engineering/

Diploma in Information Technology

Full Marks: 80

Year/Part:

II/I (2022)

© Arjun

Pass Marks: 32


Subject:

Digital Logic

Time: 3 hrs.

Candidates are required to give their answers in their own words as far as practicable. The figures in the margin indicate full mark-

Attempt ALL questions.

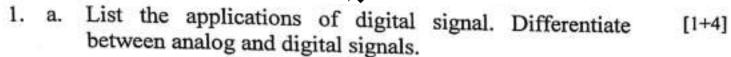

b. Convert the following:

[4×2]

- i. (257.526)₁₀=(?)₁₆
- ii. (1011001.100)₂=(?)₈

www.arjun00.com.np

- iii. (425.18)₁₀=(?)₂
- iv. (AB.2AC)₁₆=(?)₁₀
- c. Subtract 1011 from 101 using 2's complement method.

[5]

[1+3]

- a. Perform (11001+11100)₂, subtract (350)₂ from (25)₁₀ using 9's complement method.

[1+5]

[6]

What are basic gates? Explain the universality of NOR gates with figures.

OR

- State and prove De-Morgan's theorem with truth table and figures.
- Describe OR and XOR gates with truth table, symbol and logical expression.

OR

- Describe NOT and XNOR gates with truth table, symbol [1+3] and logical expression.
- a. What do you mean by Boolean algebra? Simplify the [2+3+3] following Boolean expression.
 - i. (A + B) (A + C)
- ii. $AB(\bar{B}C + AC)$

Cont.

b. Simplify the following expression using k-map. i. $F(A, B, C, D) = \sum m(0, 1, 2, 3, 7, 8, 9, 10, 11) + \sum d(6, 14, 15)$ ii. $F(A, B, C) = \pi(0, 2, 4, 6)$

 a. What is combinational logic circuit? Design a 1 to 4 [1+4] de-multiplexer with circuit diagram.

OR

Design a decimal to binary encoder with circuit diagram [5] and truth table.

Explain the operation of full adder circuit with truth table and logic diagram.

a. Define encoder. Design BCD to decimal decoder with [1+5] circuit diagram and truth table.

b. What is flip flop? Explain T-flip flop with its truth table. [1+4]

6. Write short notes on: (any TWO)

Ripple counter

b. Seven segment display

c. SIPO shift register

d. Ring counters

Good Luck!





Office of the Controller of Examinations Sanothimi, Bhaktapur

	Sanothimi, Bhaktapur Back Exam-2080 Mangsir/Poush (Scholarship)		
Yes	ogram: Diploma in Information Technology Full Ma ar/Part: I/II (2016) © Arjun Time	Pass Marks: 32 Time: 3 hrs.	
Cand	edates are required to give their answers in their own words as far as practical	ble. The	
ngur c	www.arjun00.0	om.np	
1.	Define analog and digital signal in short. Mention the advantages of digital signal over analog signal.	[4+4]	
2	Explain binary number system. Convert the following:	[2+6]	
2.	i. (1011) ₂ =(?) ₁₀ ii. (37) ₁₀ =(?) ₂ iii. (BAF) ₁₆ =(?) ₁₀	-77-21	
3.	Explain D-flip flop and T flip flop with their truth table.	[4+4]	
4.	Define shift registers. Explain SISO and SIPO shift registers.	[2+6]	
5.	What are counters? Explain ripple counter.	[2+6]	
6.	What are decoders? Explain 4 to 1 multiplexer and 1 to 4 demultiplexer.	[2+3+3]	
7.	Perform the following: i. (1000) ₂ +(1101) ₂ iii. (101) ₂ -(01) ₂ iii. (1011) ₂ ×(101) ₂	[4×2]	
8.	What do you mean by logic families? Introduce TTL, ECL and RTL families in short.	[2+6]	
9.	What do you mean by universal gates? Explain the universal properties of NAND gate.	[2+6]	
10.	Minimize the following expression: $F = \sum m (0,7,8,9,10,12) + \sum d (2,5,13); \text{ using k-map.}$	[8]	
11.	Differentiate combinational and sequential logic circuit with example. Explain 7-segments display.	[4+4	
12.	Write shot notes on: (any <u>TWO</u>)	[2×4	
	a. Full Adder b. SOP and POS www.arjun00.com. c. Alphanumeric Code	np	

Good Luck!

Master Slave JK flip flop

d.

Office of the Controller of Examinations

Sanothimi, Bhaktapur

Regular/Scholarship Exam-2080 Bhadra

Diploma in Information Technology/ Program:

Computer Engineering

Full Marks: 80

Year/Part: II/I (2022)

© Arjun

Pass Marks: 32

Subject: **Digital Logic**

Time: 3 hrs.

Candidates are required to give their answers in their own words as far as practicable. The figures in the margin indicate full marks. www.arjun00.com.np

- Define signal. Differentiate between analog and digital signal [1+3] 1. with suitable example.
 - Convert the following number system: b.

 $[4 \times 2]$

 $(10111.01)_2 = (?)_{10}$ i.

- ii. $(3471)_8 = (?)_{16}$
- iii. (BCDE.4A)₁₆=(?)₈
- iv. $(3567.350)_{10} = (?)_2$
- Perform the following operation: C.

[2×2]

- Multiply: (11101.11*101)2
- (110100.110/110)2 Divide:
- Subtract the following (11001100)₂ from (11110000)₂ using 2. a. [4] 2's complement.
 - Realize basic gate using NAND gate only with clear diagram b. [4+4]and truth table. Also, state and prove De-Morgan's Theorem in brief.
 - Explain XOR and NOR gate with truth table and symbol. C. [4]
- Simplify the following expression using Boolean algebra: 3. a. [4×2]
 - i. A'B'C' + A'BC' + AB'C' + ABC' = C'
 - ii. A(A' + C)(A'B + C)(A'BC + C') = 0
 - Simplify the following expression using k-map. b. [4×2]
 - i. $\sum f(A, B, C, D) = \pi M(2, 3, 4, 5, 7, 10, 11, 14) + \sum d(0, 1, 6, 15)$ Draw logic diagram.
 - ii. $\sum f(A, B, C, D) = \sum m(0, 1, 4, 8, 11, 12, 15) + \sum d(2, 3, 5, 6, 7)$ Draw logic diagram.
- 4. Define encoder. Explain the decimal to binary encoder with [2+6] suitable diagram and truth table.

www.arjun00.com.np

Cont. ...

	b.	Differentiate between combinational and sequential circuit with example.	[4]
	c.	Design 1:4 De-multiplexer with clear circuit diagram and truth table in brief.	[4]
5.	a,	Design RS flip-flop with necessary diagram. Write the advantages of JK flip-flop.	[6+2]
	b.	Define shift register. Explain the operation of ripple counter with clear diagram.	[2+6]
6.	Wı	rite short notes on: (any FOUR)	[4×4]
	a.	7 segments display	
	b.	SIPO shift register	
	c.	D flip-flop	
	d.	Half adder	

Good Luck!


ASCII code

BCD code

f.





 

Office of the Controller of Examinations

Sanothimi, Bhaktapur

Regular/Back Exam-2079, Phagun/Chaitra

Program: Diploma in IT Engineering Full Marks: 80 Year/Part: Pass Marks: 32 I/II (2016)

Digital Logic © Arjun Time: 3 hrs. Subject:

Candidates are required to give their answers in their own words as far as practicable. The figures in the margin indicate full marks. **www.arjun00.com.np**

Attempt any FIVE questions.

- 1. a) Define signal. Differentiate between analog and digital signal [1+3]with suitable example.
 - b) Convert the following number system: $[4 \times 2]$
 - i. $(2567.350)_{10} = (?)_2$
 - ii. (BCDE .4A)₁₆ = $(?)_8$
 - iii. $(1100110011)_2 = (?)_{16}$
 - iv. $(376.351)_8 = (?)_{10}$
 - c) Perform the following operation: [2×2]
 - Divide: (1100110011)₂ /(1011)₂
 - ii. Multiply: $(1011001101)_2 \times (101101)_2$
- 2. a) State and prove De-Morgan's Theorem with necessary [8] diagram and truth table.
 - b) Simplify the following expression using Boolean Algebra. [2×4]
 - i. Z(Y+Z)(X+Y+Z)=Z
 - ii. A'BC + AB'C + ABC + BC'
- a) Simplify the following expression using k-map. [2×4]
 - i $\sum F(A, B, C, D) = \pi m(2,3,4,5,7,10,11,14) + \sum d(0,1,6,15)$
 - ii. $\sum F(A, B, C, D) = \sum M(0,1,4,8,11,12,15) + \sum d(2,3,5,7)$
 - b) Realize basic gate using universal NAND gate only with [8] truth table and logic circuit.
- 4. a) Define multiplexer. Explain the operation of full subtractor [2+6]with clear logic diagram, truth table and expression.

Cont.....

- b) Define encoder. Design and explain seven segment Display [2+6] decoder with necessary diagram and truth table.
- a) Define counter, Explain the operation of "I" flip flop with [2+6] necessary diagram and truth table.
 - b) Define adder. Explain about ripple counter with necessary [2+6] diagram.

 © Arjun
- 6. Write short notes on: (Any Four)

 $[4\times4]$

- a) ASCII Code
- b) DTL Logic Family
- c) AND & OR Gates
- d) 1:4 De-multiplexer
- e) SISO Shift Register

Good Luck!





Council for Lechnical Education and Vocational Training Office of the Controller of Examinations Sanothimi, Bhaktapur Regular/Back Exam-2078, Magh/Falgun Program: Diploma in Computer Engineering Full Marks:80 Year/ Part: I/II (2018) © Arjun Pass Marks: 32 Digital Logic Time: 3 hrs. Candidates are required to give their answers in their own words as far as practicable. The figures in the margin indicate full marks. www.arjun00.com.np Attempt Any Five Questions. Differentiate analog and digital signals. What do you [6+2]mean by positive and negative logic. b) Perform following task: [4x2] i Convert (41.6875)₁₀ into binary ii Convert (1001)2 into BCD iii Convert (1011)2 into decimal IV Convert (12AB)₁₆ into decimal a) Explain about basic gates with necessary truth table and [8] logical expression. b) Explain universal gates and why are they called so? [2+6]Reduce the following expression using k-map. $F(A,B,C,D_i) = \sum_{i=1}^{n} (0,1,2,4,5,6,8,9,12,13,14)$ a) State and prove De-Morgan theorem using troth table and [5+3]b) Explain the working of 8 to 1 multiplexer with necessary [6+2][2+6]of Boolen Algebra. [6+2]

3. logic diagram. Subtract (11101010)2 from (11111000)2 using 2's complement.

diagram and truth table. What do you mean by combinational logic circuit?

 a) Define Boolen Algebra. State and explain basic properties 4.

 b) Design BCD to Decimal decoder with necessary diagram and truth table and mention different types of decoder IC package.

a) Define latch and flip-flop. Explain JK flip-flop with all [2+6]5. necessary diagram; symbol, truth table.

b) Explain Ripple up counter with timing diagram.

[4x4=16] Write short notes on : (Any Four) 6.

i) SISO shift register

ii) LCD display

[8]

iii) 7- Segment Display

iv) Half adder www.arjun00.com.np

v) Alphanumeric code

Subject:

1.

2

Good Luck!

Office of the Controller of Examinations

Sanothimi, Bhaktapur

Regular/Back Exam-2077, Chaitra

Program:

Diploma in Computer Engineering

Full Marks: 80

Year/Part:

I/II (2018 New Course)

Pass Marks: 32

Subject:

Digital Logic

© Arjun

Time: 3 hrs

Candidates are required to give www.arjun00.com.np

Attempt Any Eight questions.

- Differentiate between Analog and digital signal with [5+5]1. example. Give brief description about types of number system.
- Perform the following: 2.

[5x2=10]

i) $(625.25)_{10} = (?)_2$

- ii) $(12AB5)_{16} = (?)_2$
- iii) $(1001101)_2 = (?)_8$
- iv) $(111000)_2 = (?)_{10}$
- $v) (101000110)_2 = (?)_{15}$
- about 9's 10's [2+4+4] Define complement. Describe and 3. complement with suitable example.
- Explain briefly about basic gates. Prove that NOR gate as [5+5]4. universal gate!
- State and prove De-Morgan's theorem. Differentiate 5. [5+5]between sum of product (SOP) and product of sum (POS).
- Define algebra with its laws. Simplify the fallowing using [4+6]6. K-map:

 $F(A,B,C,D) = \Sigma (1,2,4,7,10,12,14) + \Sigma d (6,8,11,13)$

- What do you mean by Decoder? Design a Decimal to BCD [3+7]7. encoder with necessary logic diagram.
- Elaborate about JK and masters-lave flip-flop with its [5+5]8. symbol and truth table.
- 9. Compare between synchronous [5+5]and Asynchronous counter. Explain about SIPO shift register in brief.
- 10. Write short notes on : (Any Two)

[2x5=10]

- a) Gray Code
- b) 4-to-1 multiplexer
- d) 7-segment display c) Ring Counter
- e) Half Adder

Good Luck!

www.arjun00.com.np

Council for Technical Education and Vocational Training Office of the Controller of Examinations Sanothimi, Bhaktapur Regular/Back Exam-2076, Shrawan/Bhadra program: Diploma in Computer Engineering Year/Part: Full Marks: 80 I/ II (2018) © Arjun Pass Marks: 32 Subject: Digital Logic Time: 3 hrs Candidates are required to practicable. The figures in the www.arjun00.com.np Attempt Any Five questions. 1. a) What do you mean by Propagation delay and Noise [4] Margin? Convert the following: [2x4=8] (i) (625.256)₁₀ $=(?)_2$ (iii) $(101101.110)_2 = (?)_{10}$ (ii) $(101110.101)_2 = (?)_8$ (iv) (256.625)₁₀ $= (?)_{16}$ c) Subtract10111 from 10011 using 2's complement. [4] Why we use NOR gate as AND, OR and NOT gate. [6] b) State and prove De-Morgan's theorem with suitable [6] diagram and truth table c) Prove using Boolean Expression. (A+B) (A+C) = A+ BC [4] 3. a) Simplify Boolean expression by using logic diagram: [6] Y = ABCD + ABCD + ABC + ACDb) Simplify using K-map in SOP & POS form: F(A, B, C, D) = [6] $\sum m (0, 2, 3, 4, 5, 10, 11, 15) + \sum d (1, 6, 9, 13).$ c) Compare between combinational logic and sequential logic [4] circuit. 4. a) Define Adder. Explain the full subtractor with truth table [8] and logic diagram. b) Design a 8:1 MUX with its symbol, truth table and logic [8] diagram. 5. a) Describe the operation of R-S flop-flip with diagram and [4] necessary table. b) Explain about PIPO shift register. [4] c) Define Flip-flop. Describe about ripple counter. [2+6]4x4=16] Write short notes on: (Any Four) 6. d) Encoder a) BCD code e) Ring counter b) Master -slow Flip-flop c) Seven segment display www.arjun00.com.np Good Luck!

Council for Technical Education and Vocational Training Office of the Controller of Examinations Sanothimi, Bhaktapur

Regular/ Back 2075 Shrawan / Bhadra

Program: Diplome in Computer Engineering / Full Marks: 80 Information Technology Pass Marks: 32 Year/ Part: I/II(DIT old Course) Subject: Logic Circuit © Arjun Time: 3 hrs. www.arjun00.com.np Candidates are requir far as practicable. Th Attempt (All) Questions. Differentiate between analog and digital signal with [2+2] 1. example. [22] Convert the following. **(b)** (1234)₁₀ into binary (10110101.01011), in to decimal Convert the following number system as indicated: [10] 2. (a) $(11011.101)_2 = (?)_{10}$ Subtract / 11011 from 11001010 suing **[3**] (b) complement method What is NAND gate? Draw it's symbol, Write the true 3. (a) 161 table and logic equation for it. State and prove the De-Morgan's theorem with necessary (b) 161 table and diagram. Simplify using k-map in sum product (SOP) and product 4. (a) [3+3] of sum (POS) from. $F(A,B,C,D) = \Sigma(1.5,12,14,15)$ and don't care condition. $D(A,B,C,D) = \sum (0,3,4,6,10)$. **(b)** Differentiate between combinational logic circuit and [6] sequential logic circuit www.arjun00.com.np 5. (2) Explain about Half adder and half adder SOL -[8] stractors' with examples. Contd.....

(b) Prove the following equation by using Boolean algebra. I) X×X=X II) X+XY=X

[203]

OR

Design a 3 bits combination of circuit whose output Y = 1 when the input binary is greater than or equal to 6.

 (a) Simplify the following expression and realize it using [8] different gates.

AB'C+AB+AD'+ABCD+AC'.

OR

What is a Decoder? Explain BCD to seven segment decoder with truth table

(b) Explain the T Flip-Flop with logic diagram and necessary tables.

[6]

 (a) Define multiplexer. Explain about the serial in serial [4+2] out shift register.

OR

Define counter. Explain about Ripple counter with diagram.

(b) Write short notes (any three)

[3×3=9]

- i. Gray Code
- ii. Universal Gate
- iii. 1-4 De-multiplexer
- iv. LCD display

Good kuck !





Council for Technical Education and Vocational Training Office of the Controller of Examinations Sanothimi, Bhaktapur Regular/Back Exam-2074, Shrawan/Bhadra Program: Diploma in Computer Engineering Full Mark: 80 Year/Part: I/II Pass Mark: 32 © Arjun **Logic Circuits** Subject: Time: 3 hrs. www.arjun00.com.np Candidates are require as practicable. The figure Attempt any ten Questions. Differentiate between analog and digital signal. [4+4] Explain the applications of digital signal. Explain Octal and Hexadecimal number system. [4+4] Convert following numbers into specified number system. $a)(101)_{10} = (?)_2$ $b)(564)_8 = (?)_{16}$ Divide (1011010)₂ by (111)₂. Subtract (1101)₂ to [4+4] (111)₂ using 2's complement method. Explain AND, OR and NOT gates with its truth [6+2]table and gate diagrams. What are universal gates? Explain. Define Boolean Algebra and write down its [3+5]properties. Explain DeMorgan's Theorems. Explain K-Map simplification for two input variable [8] and three input variable with example. Explain Half adder and full adder logic circuits with [8] its combinational circuit diagram. What are decoders? Explain 4-to-1 multiplexer and [2+6]1-to-4 demultiplexer. Explain RS Flip-Flop and JK Flip-Flop with their [8] truth table. Define shift registers. Explain SISO and SIPO shift [2+6]10. registers. What are counters? Explain Ripple counters. Write [2+3+3]11. down the applications of counters. Write short notes on: (Any two) [4*2=8] 12. a. LCD display b. Applications of Flip-Flop www.arjun00.com.np c. Encoders d. Alphanumerical display Good Luck!

1.

2.

3.

4.

5.

6.

7.

8.

9.

Office of the Controller of Examinations

Sanothimi, Bhaktapur

Regular/Back Exam-2073 Bhadra/Ashwin

Program: Diploma in Information Technology

Full Mark:60

/Computer Engineering

Year/Part: I/II(New Course)

Pass Mark:24

Subject:

Logic Circuits

© Arjun

Time: 3 hrs.

Candidates are required to c www.arjun00.com.np



Attempt Any Five (5) Questions.

[2+4=6]	a) Define Signal. Differentiate between analog and digital signal with suitable example.	1
[1x4=4]	b) Convert the following number system. i. (2564.87D) ₁₆ = (?) ₂ ii. (4432.123) ₈ = (?) ₁₆ iii. (111101010*11010) ₂ iv. (1101001.110) ₂ / (110) ₂	
[2]	c) Subtract the following (11101010) ₂ from (111110000) ₂ using 2's Compliment.	
[3+3]	a) Explain about AND and OR gate with necessary truth table, symbol and logical expression.	2.
[1+5]	 b) Define Universal gate. Explain how NOR gate operate as Basic gate with necessary realization technique. 	
[6]	a) Simplify the following expression using K- map. ΣF(A,B,C,D)= Σm(0,1,3,4,7,8,12,15) Σd (2,5,6,14)	3.
[1+5]	 b) Define Adder. Explain the operation of Full adder with clear diagram and truth table. 	
[1+5]		4.
[6]	 b) Design 8:1 Multiplexer with clear circuit diagram and truth table. 	
[1+5]	a) Define Flip-flop. Explain the operation of JK flip flop with necessary diagram and truth table.	5.
[1+5]	 b) Define counter. Explain the operation of ripple counter with clear diagram 	

www.arjun00.com.np

6.	Write short notes on : (Any Four)	[4x3=12]
	a) LCD display b) SISO shift register c) Gray code d) De Morgan's theorem e) Demultiplexer	





Council for Technical Education and Vocational Training Office of the Controller of Examinations Sanothimi, Bhaktapur

Regular/ Back Exam 2072, Bhadra/Ashwin

Program : Diploma in Computer Engineering Full Marks: 80

(New Course)

Year/ Part : I/II

© Arjun

Pass Marks: 32

Subject

: Logic Circuits

Time: 3 hrs.

Candidates are required to give www.arjun00.com.np

Attempt (Any Eight) Questions.

- [10] Explain the importance of digital signal over analog 1. signal with examples.
- (a) Discuss about the different number system in brief. [5] 2.
 - [5] Convert (AB.52) to into Octal number. (b)
- [5+5=10] What is BCD code? Write on the alpha numeric 3. code.
- [4+6=10] Why NAND and NOR gates are called universal 4. gates? Realize the basic logical gate using NAND gate.
- What is K-map? Explain sum of product and product 5. of sum simplification. [4+3+3=10]
- [10] Design a decimal to BCD decoder with diagram. 6.
- [2+8=10] 7. What is multiplexing? Design 8:1 multiplex with neat sketch diagram.
- [2+8=10]Define the term "flip-flop". Explain different types of 8. flip-flop in brief. www.ariun00.com.np
- Writhe short notes on: (Any Two) [2x5=10] 9.
 - a) SISO shift register
 - b) Decade counter
 - c) LED display
 - d) 2's complement method.